

Figure 1: Simple circuit with a battery and resistors.

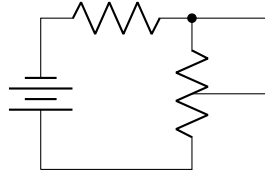


Figure 2: Simple circuit with a battery and resistors.

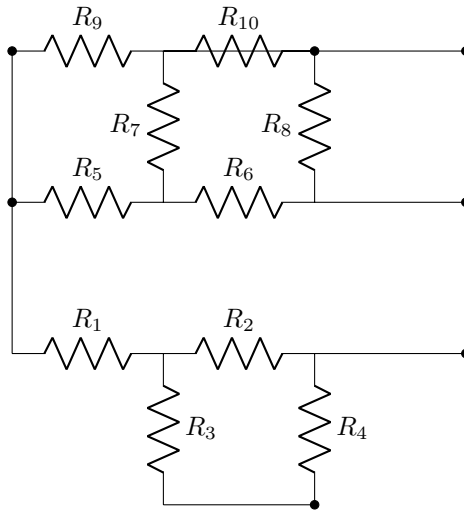


Figure 3: Complex resistor network.

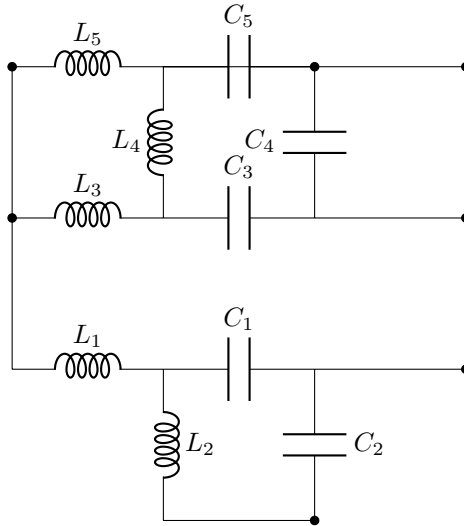


Figure 4: Inductor and capacitor network.

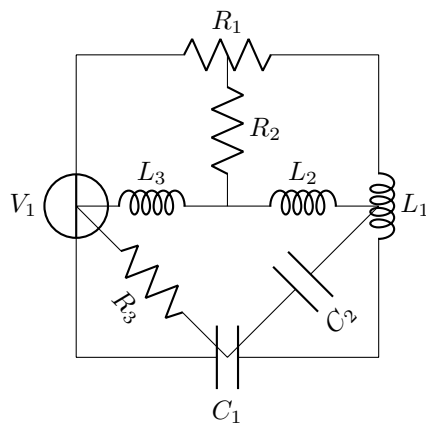


Figure 5: Complex circuit with voltage source, resistors, inductors, and capacitors.